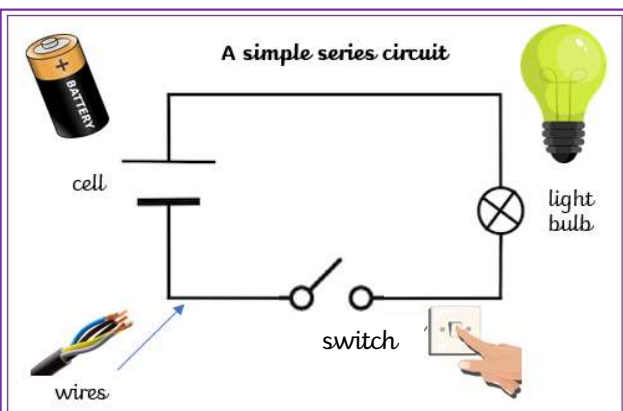


## What I already know




Closing the switch completes the circuit and electricity will flow.

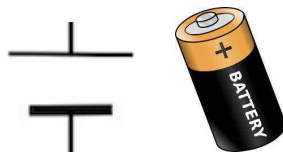
## Year 6 electricity Knowledge organiser




**Cell** – also called a **battery**. Gives electrical power to the circuit



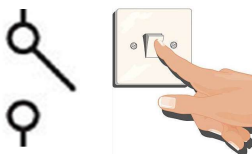
**switch** – allows us to control the circuit. If it is closed the electricity will flow. If it is open the electricity will stop.



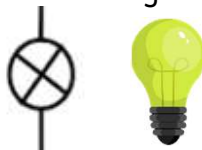
**bulb** – it creates light when electricity flows through it.



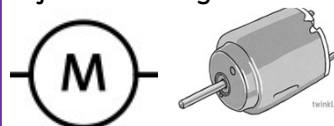**motor** – It moves when electricity flows through it.




## What I will learn in this enquiry

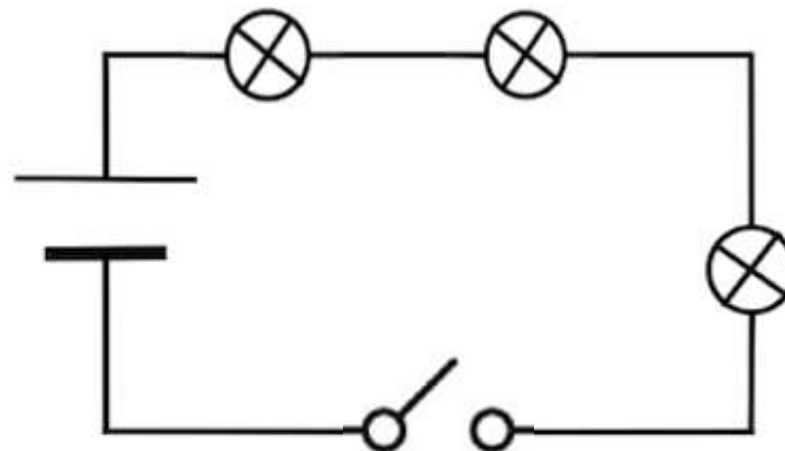


The brightness of the bulb (or the loudness of a buzzer) will change depending on **how many bulbs** (or **buzzers**) or **cells** are in the circuit.

### electrical conductors

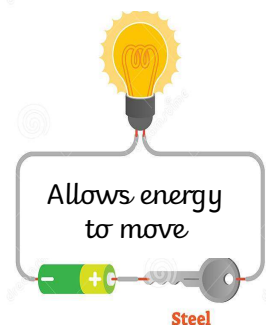

### electrical insulators

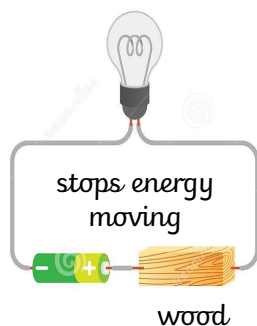

VS



cell



wire



bulb



buzzer



motor



switch (off)



switch (on)

Circuit diagrams use these symbols to avoid confusion